

## 4. References

### Voltage or Current References

Circuit that yields a precise DC voltage or current independent of external influences is called a voltage reference or a current reference.

The primary external influences are:

- Power supply variations
- Temperature variations

### Sensitivity and Fractional Temp. Coefficient

Used to characterize the dependence of a reference on power supply and temperature.

A. The Sensitivity of  $V_{ref}$  to changes in power supply  $V_{DD}$  is given by,

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} \quad (1)$$

$$\text{Or, } \frac{\partial V_{ref}}{V_{ref}} = S_{V_{DD}}^{V_{ref}} \cdot \frac{\partial V_{DD}}{V_{DD}} \quad (2)$$

### Sensitivity

Sensitivity may vary from 0.0 to 1.0.

Sensitivities less than 0.01 are practical values for a monolithic voltage reference.

The above formulation is valid for current references by simply replacing  $V_{ref}$  by  $I_{ref}$ .

### Fractional Temp. Coefficient

B. The Sensitivity of  $V_{ref}$  to changes in temperature  $T$  is given by,  $S_T^{V_{ref}}$

$$S_T^{V_{ref}} = \frac{T}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

Got just by replacing  $V_{DD}$  by  $T$  in eqn (1)

$$\text{Or, } \frac{\partial V_{ref}}{V_{ref}} = S_T^{V_{ref}} \cdot \frac{\partial T}{T}$$

### Fractional Temp. Coefficient

Fractional Temp. Coefficient,  $TC_F(V_{ref})$ :

This is another popular concept used to measure the degree of temperature dependence of reference.

$$TC_F(V_{ref}) = 1/V_{ref} (\partial V_{ref}/\partial T) = 1/T (S_T^{V_{ref}})$$

Units of  $TC_F$  - parts per million/ $^{\circ}\text{C}$  or ppm/ $^{\circ}\text{C}$ .

Example:

Sensitivity,  $S_T^{V_{ref}} = 0.01$  at room temperature,  
 $\Rightarrow TC_F(V_{ref}) = 1/T (S_T^{V_{ref}})$   
 $= (1/300) \times 0.01 \times 1,000,000$   
 $= 33.3 \text{ ppm/}^\circ\text{C}$

References with  $TC_F$  of less than 50ppm/ $^\circ\text{C}$  are considered to be stable w.r.t. temperature.

**Simple Voltage References**


In CMOS IC design, we can derive reference voltages from the power supplies using resistors and MOSFETs.

1. Resistor – Only Voltage Reference
2. Resistor – MOSFET Voltage Reference
3. MOSFET – Only Voltage Reference

**1. Resistor – Only Voltage Reference**

This voltage divider, formed with 2 resistors, provide a DC voltage between  $V_{DD}$  and ground depending on values of  $R_1$  and  $R_2$ .

Here,  $V_{ref} = \frac{R_2}{(R_1 + R_2)} V_{DD}$

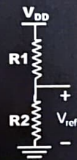**Advantages:**

- Simple
- Temperature Insensitive
- Process Insensitive – changes in the sheet resistance have no effect on the voltage division.

**Disadvantages:**

- To reduce the power dissipation, the resistors must be made large. But large resistors require a large die area.
- The sensitivity of  $V_{ref}$  w.r.t.  $V_{DD}$  is found to be,

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = 1$$

**2. Resistor – MOSFET Voltage Reference**

Since gate and drain terminals are shorted,  $M_1$  always remains in saturation.

Here,  $V_{DS} = V_{GS} = V_{ref}$

$$I_D = (V_{DD} - V_{ref})/R = \frac{1}{2}\beta_1(V_{GS} - V_{th})^2$$

Or,  $V_{ref} = V_{th} + \sqrt{\frac{2I_D}{\beta_1}} = V_{th} + \sqrt{\frac{2(V_{DD} - V_{ref})}{R\beta_1}}$

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = \frac{1}{V_{th} \sqrt{\frac{2R\beta_1}{V_{DD}}} + 2}$$



$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \left[ \frac{\partial V_{th}}{\partial T} - \frac{1}{2} \sqrt{\frac{2V_{DD}}{R\beta_1}} \left( \frac{1}{R} \frac{\partial R}{\partial T} - \frac{1.5}{T} \right) \right]$$



### 3. MOSFET – Only Voltage Reference


This generates a reference voltage equal to the voltage on the gates of the MOSFETs w.r.t. ground.

$$\frac{1}{2}\beta_1(V_{ref}-V_{SS}-V_{th})^2 = \frac{1}{2}\beta_2(V_{DD}-V_{ref}-V_{th})^2$$

Or the reference voltage is given by,

$$V_{ref} = \frac{V_{DD} - V_{th} + \sqrt{\frac{\beta_1}{\beta_2}}(V_{SS} + V_{th})}{\sqrt{\frac{\beta_1}{\beta_2}} + 1}$$
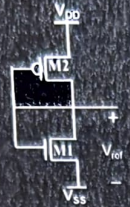
$$\frac{\beta_1}{\beta_2} = \left[ \frac{(V_{DD} - V_{ref} - V_{th})^2}{(V_{ref} - V_{SS} - V_{th})^2} \right]$$



Sensitivity of  $V_{ref}$  w.r.t.  $V_{DD}$  is given by,

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = \frac{V_{DD}}{V_{DD} - V_{th} + \sqrt{\frac{\beta_1}{\beta_2}}(V_{SS} + V_{th})}$$

Assuming the temperature dependence of the ratio of the transconductance parameters,  $\beta_1/\beta_2$ , is negligible, the  $TC_F(V_{ref})$  is given by,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[ \frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right]$$

To achieve  $TC_F(V_{ref}) = 0$  requires,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[ \frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right] = 0$$

$$\text{i.e., } \frac{\partial(-V_{th})}{\partial T} = -\sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \Rightarrow 2.7 \text{ mV}/^\circ\text{C} = \sqrt{\frac{\beta_1}{\beta_2}} (2.4 \text{ mV}/^\circ\text{C})$$

$$\text{i.e., } \beta_1/\beta_2 = 1.125$$

Zero temperature coefficient, to a first order can be met by satisfying this equation. However, this ratio is most often set by the desired  $V_{ref}$ . So for a particular single value of  $V_{ref}$ , the reference becomes temperature insensitive.

#### Design Example:

Design a 3V MOSFET-Only voltage reference. Determine the temperature coeff. of the reference. Data given:  $V_{DD}=+5\text{V}$ ,  $V_{SS}=0\text{V}$ ,  $V_{th}=0.8\text{V}$ ,  $V_{th}=0.9\text{V}$ ,  $L_1=L_2=5\mu\text{m}$ ,  $K_n=50\mu\text{A/V}^2$ ,  $K_p=17\mu\text{A/V}^2$ .

$$\frac{\beta_1}{\beta_2} = \left[ \frac{(5 - 3 - 0.9)^2}{(3 - 0 - 0.8)^2} \right] = 0.25$$

Setting  $L_1=L_2=W_1=5\mu\text{m}$ ,

$$\frac{\beta_1}{\beta_2} = \frac{K_n W_1 L_2}{K_p W_2 L_1} = \frac{50\mu\text{A/V}^2 \cdot 5\mu\text{m} \cdot 5\mu\text{m}}{17\mu\text{A/V}^2 \cdot W_2 \cdot 5\mu\text{m}} = 0.25$$

Solving gives,  $W_2 = 60\mu\text{m}$ .

The temp. coeff. is given by,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[ \frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right]$$

$$\text{But, } \frac{\partial V_{th}}{\partial T} = V_{th} \cdot TC_{V_{th}} = (0.8\text{V})(-0.003/^\circ\text{C}) = -2.4 \text{ mV}/^\circ\text{C}$$

$$-\frac{\partial V_{th}}{\partial T} = -V_{th} \cdot TC_{V_{th}} = -(0.9\text{V})(-0.003/^\circ\text{C}) = 2.7 \text{ mV}/^\circ\text{C}$$

$$TC_F(V_{ref}) = \frac{1}{3} \cdot \frac{1}{\sqrt{\frac{50 \times 5}{17 \times 60}} + 1} \left[ 0.0027 + \sqrt{\frac{50 \times 5}{17 \times 60}} (-0.0024) \right] = 337 \text{ ppm}/^\circ\text{C}$$

### Current Source Self-Biasing Circuits

The drawback of the 3 references discussed so far are that, they are very sensitive to power supply and temperature.

Here, we discuss 3 methods of biasing which reduce the effects of power supply variations and possibly temp.

1. Threshold Voltage Referenced Self-Biasing
2. Diode Referenced Self-Biasing
3. Thermal Voltage Referenced Self-Biasing



## 1. Threshold Voltage Referenced Self-Biasing


MOSFETs M3 & M4 force the same current to flow through M1 & M2.

$$IR = V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$

If  $\beta_1$  is very large, then,  $I$  is given by,

$$I \approx V_{TN}^2/R$$

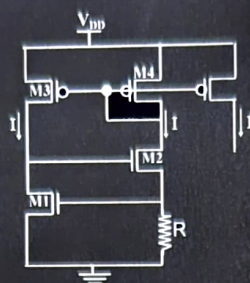i.e., current is independent of the power supply voltage (neglecting channel length modulation and body effect).




$$I = \frac{1}{2}\beta_1(V_{GS1} - V_{TN})^2$$

$$\text{Or, } V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$


### Note:

- Here we assumed the output resistance of the MOSFET were infinite. But by cascoding M3 and M4 helps to make the bias circuit behave more ideal.
- The accuracy of  $I$  is limited by the threshold voltage accuracy, which may vary by 20%, and the  $n+$  resistivity, which may vary by 20% as well.
- $TC_F(I)$  depends on  $TC_F(V_{TN})$  and  $TC_F(R)$ . But  $TC_F(V_{TN}) = -3000 \text{ ppm}/^\circ\text{C}$  and  $TC_F(R) = +2000 \text{ ppm}/^\circ\text{C}$ . So, the reference current,  $I$  has a large negative temperature coefficient.

## Startup Circuit

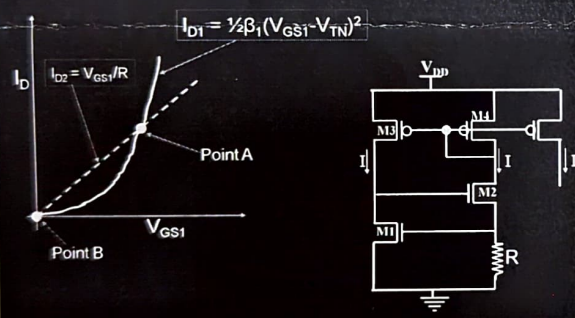


## Startup Circuit

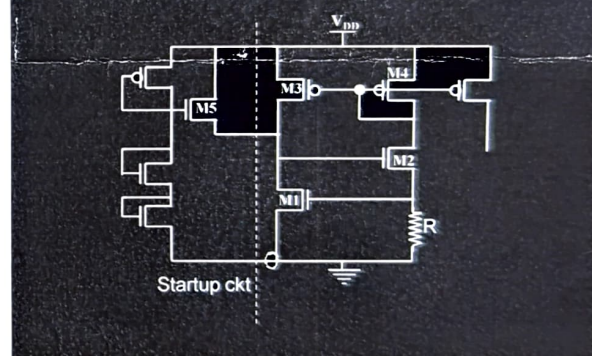
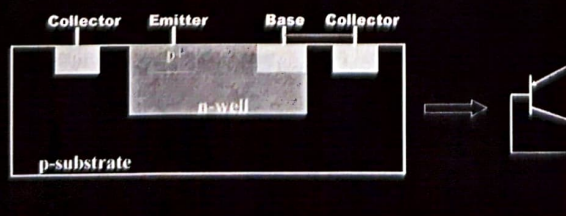
## 2. Diode Referenced Self-Biasing

The parasitic PNP transistor, available in the  $n$ -well process, in conjunction with the CMOS transistors, is used to generate the reference current or voltage.



A Base-Collector connected transistor is equivalent to a Diode.




The no. '1' indicates the minimum sized emitter. The current through a forward-biased Diode is given by,

$$I_d = I_s e^{V_d/V_T} \quad \text{Where } V_T \text{ is the thermal voltage} = kT/q$$

$I_s$  is the saturation current



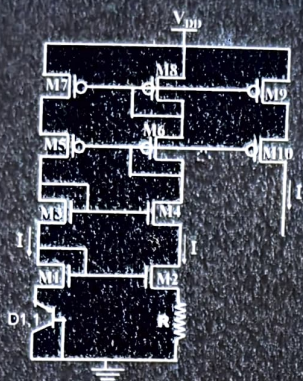

Diode Referenced Self-Biasing Circuit

Here the cascode mirrors made with M1 through M8 force the same current,  $I$ , to flow through D1 and R

$$I = V_d/R = I_s e^{V_d/\eta V_T}$$

$$\text{Or, } V_d = \eta V_T \ln(I/I_s)$$

Solving for the resistor gives,

$$R = \frac{\eta V_T}{I} \ln(I/I_s)$$

The main benefit of this circuit over the threshold referenced self-biasing circuit is the better matching, from wafer to wafer and on the same die, of the diode voltage over the threshold voltage.

### Sensitivity and $TC_F(I_{ref})$ :

$$I_{ref} = V_d/R$$

This shows that the reference is insensitive to power supply variations.

$$TC_F(I_{ref}) = \frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial T} = \frac{1}{I_{ref}} \frac{\partial}{\partial T} \left( \frac{V_d}{R} \right)$$

$$= \frac{1}{I_{ref}} \left[ R \frac{\partial V_d}{\partial T} - \frac{V_d}{R^2} \frac{\partial R}{\partial T} \right]$$

$$TC_F(I_{ref}) = \frac{1}{V_d} \frac{\partial V_d}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} = TC_F(V_d) - TC_F(R)$$


$$TC_F(I_{ref}) = TC_F(V_d) - TC_F(R)$$

Drawback: Temperature dependence.

The temp. coeff. of the diode  $\approx -3,300 \text{ ppm}/^\circ\text{C}$  and R has  $+2000 \text{ ppm}/^\circ\text{C}$ . This causes the biasing circuit to have a large negative temperature coefficient.

Therefore, this reference is also called as CTAT (Complimentary To Absolute Temperature).
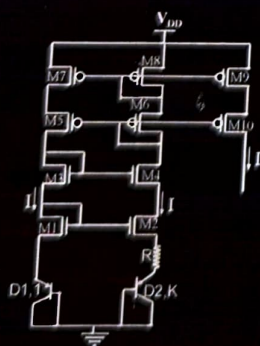
### 3. Thermal Voltage Referenced Self-Biasing



M1 through M8 forces the same current through D1 and D2.

$$V_{d1} = IR + V_{d2} \quad (1)$$

$$I_{d1} = I_s e^{V_{d1}/\eta V_T} \rightarrow V_{d1} = \eta V_T \ln \frac{I}{I_s}$$

$$I_{d2} = K I_s e^{V_{d2}/\eta V_T} \rightarrow V_{d2} = \eta V_T \ln \frac{I}{K I_s}$$

From eqn. (1), solving for the resistor, R, gives,

$$R = (V_{d1} - V_{d2})/I = \frac{\eta V_T}{I} \ln(K)$$

$$\text{Or, } I = \frac{\eta V_T}{R} \ln(K) = \frac{\eta k}{qR} \ln(K) \cdot T \quad \left| \quad V_T = kT/q \right.$$



$$\text{Or, } I = \frac{\eta V_T \ln(K)}{R} = \frac{\eta k \ln(K) \cdot T}{qR}$$

Here, the current is proportional to the absolute temperature (PTAT).

$$TC_F(I_{ref}) = \frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial T} = \frac{1}{I_{ref}} \frac{\partial}{\partial T} \left( \frac{\eta V_T \ln(K)}{R} \right)$$

$$TC_F(I_{ref}) = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} = TC_F(V_T) - TC_F(R)$$

$$TC_F(I_{ref}) = TC_F(V_T) - TC_F(R)$$

#### Advantages:

Since both  $V_T$  and  $R$  exhibit positive temperature coeff., it gives better temperature characteristics than the diode or threshold voltage references.


$TC_F(V_T) \approx +3,300 \text{ ppm}/^\circ\text{C}$ , and  $TC_F(R) \approx +2000 \text{ ppm}/^\circ\text{C}$   
Hence,  $TC_F(I_{ref}) \approx 1,300 \text{ ppm}/^\circ\text{C}$

#### Drawbacks:

Mismatches in the gate-source voltages of M1 and M2 can result in large variations in  $I_{ref}$ .
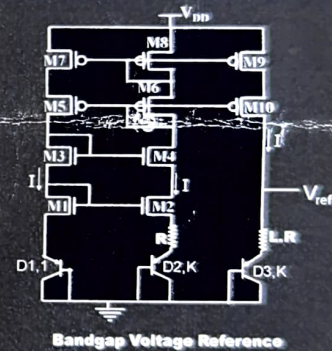
## Bandgap Voltage References

Bandgap voltage references combine the **positive TC** of the thermal voltage with the **negative TC** of the diode forward voltage in a circuit to achieve a voltage reference with a **zero TC**.



Diode D3 is the same size as D2, while the resistor in series with D3 is L times larger than the resistor in series with D2.

The current  $I$  in the figure is given by,

$$I = \frac{\eta V_T \ln(K)}{R}$$

The reference output voltage w.r.t. ground is given by,

$$V_{ref} = I \cdot L \cdot R + V_{d3}$$

$$\text{Or, } V_{ref} = (L \cdot \eta \ln(K) V_T + V_{d3} = (L \cdot \eta \ln(K) V_T + \eta V_T \ln \frac{1}{K} I_s$$

The TC of the bandgap reference is zero when,

$$\frac{\partial V_{ref}}{\partial T} = L \cdot \eta \ln(K) \frac{\partial V_T}{\partial T} + \frac{\partial V_{d3}}{\partial T} = 0$$

$$\frac{\partial V_{ref}}{\partial T} = L \cdot \eta \ln(K) \frac{\partial V_T}{\partial T} + \frac{\partial V_{d3}}{\partial T} = 0$$

$0.085 \text{ mV}/^\circ\text{C} \quad -2 \text{ mV}/^\circ\text{C}$

This is true when,


$$L \cdot \eta \ln(K) = 2/0.085 = 23.5$$

For  $\eta=1$  and  $K=8$  the factor  $L = 11.3 \approx 12$  for a zero TC.

The value of  $V_{ref}$  [for  $\eta=1, K=8, L=12, V_T=26\text{mV}, I=10\mu\text{A}, I_s=10^{-15}\text{A}, T=300^\circ\text{K}$ ] will be,

$$V_{ref} = (L \cdot \eta \ln(K) V_T + \eta V_T \ln \frac{1}{K} I_s = 1.25\text{V}$$
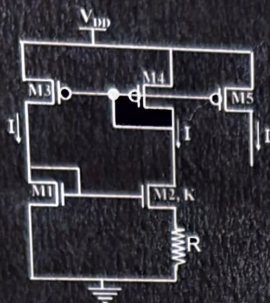
## Beta Multiplier Referenced Self-Biasing



Width of M2 is made 'K' times larger than width of M1, so that,

$$\beta_2 = K \beta_1 \text{ assuming } L_1 = L_2 \text{ and } W_2 = K W_1$$

and therefore,

$$V_{GS1} = V_{GS2} + IR \quad (1)$$

But,

$$V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$

Neglecting body effect,

$$V_{GS2} = V_{TN} + \sqrt{\frac{2I}{K \beta_1}}$$

$$I = \frac{1}{4} \beta (V_{GS} - V_{TN})^2$$

$$\text{Or, } V_{GS} = V_{TN} + \sqrt{\frac{2I}{\beta}}$$

Solving for I,

$$I = \frac{2}{R^2 \beta_1} \left[ 1 - \sqrt{\frac{1}{K}} \right]^2 \quad (2)$$

This is the basic design equation for this reference. K is always greater than 1.

Temperature coeff. of the current reference is,

$$TC_{I_{REF}} = \frac{1}{I} \frac{\partial I}{\partial T} = -2 \frac{1}{R} \frac{\partial R}{\partial T} + \frac{1}{\beta_1} \frac{\partial \beta_1}{\partial T}$$

$$= -4000 \text{ ppm}/^\circ\text{C} + \frac{1.5}{T}$$

## Biased $\beta$ multiplier reference

